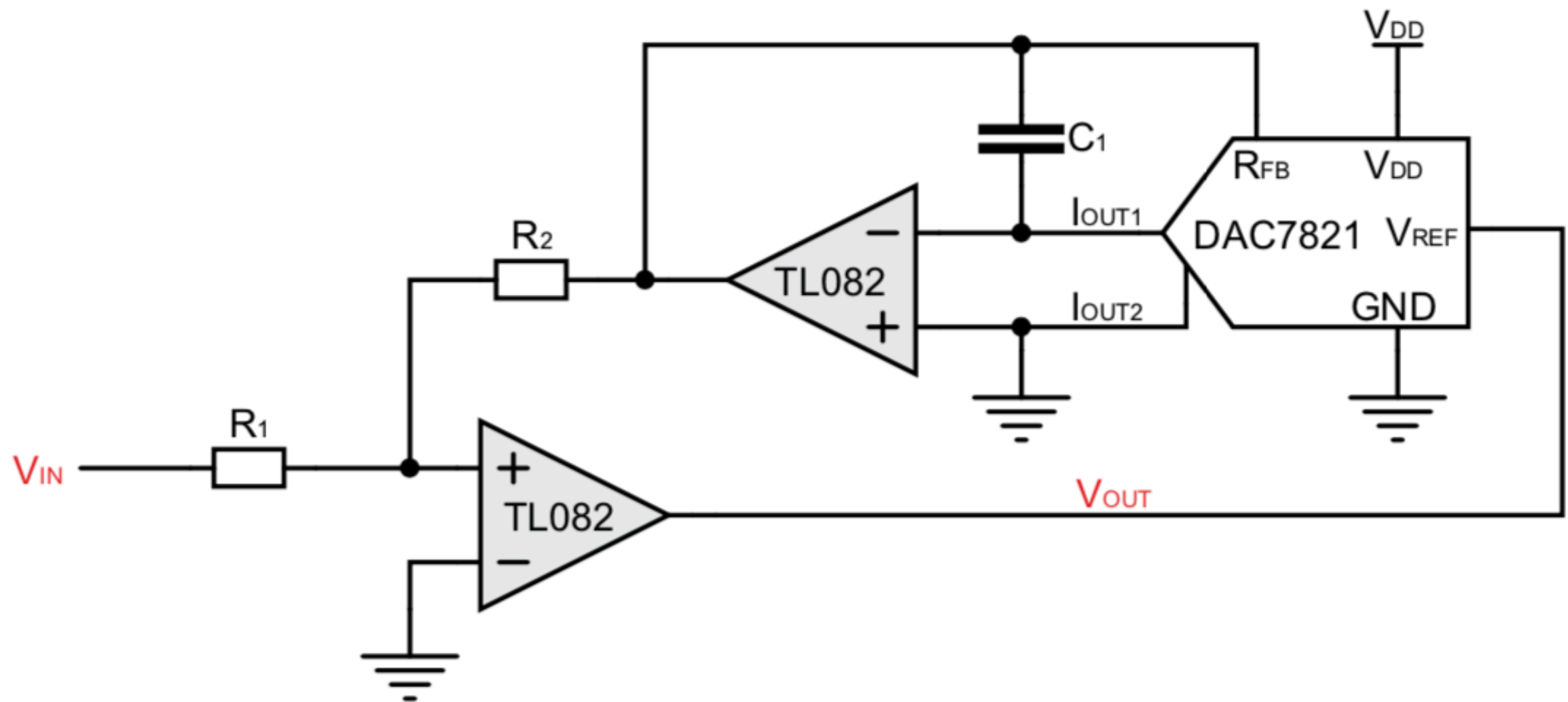



ANALOG SCHALTUNGSTECHNIK

Digital Controlled Gain Stage Amplifier


DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER



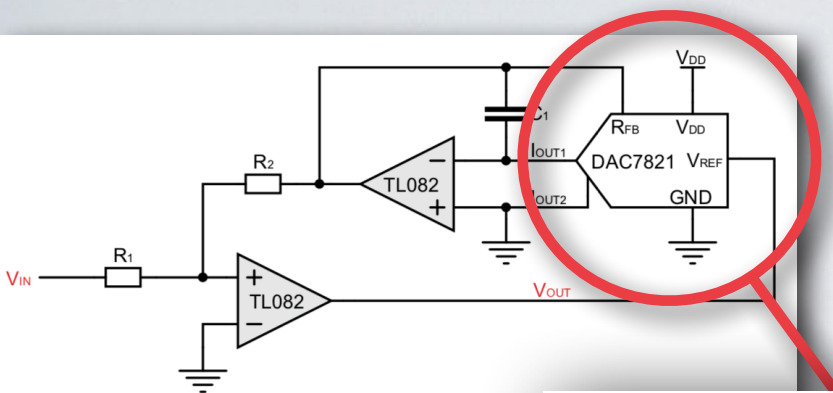DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER




Digital Analog Converter

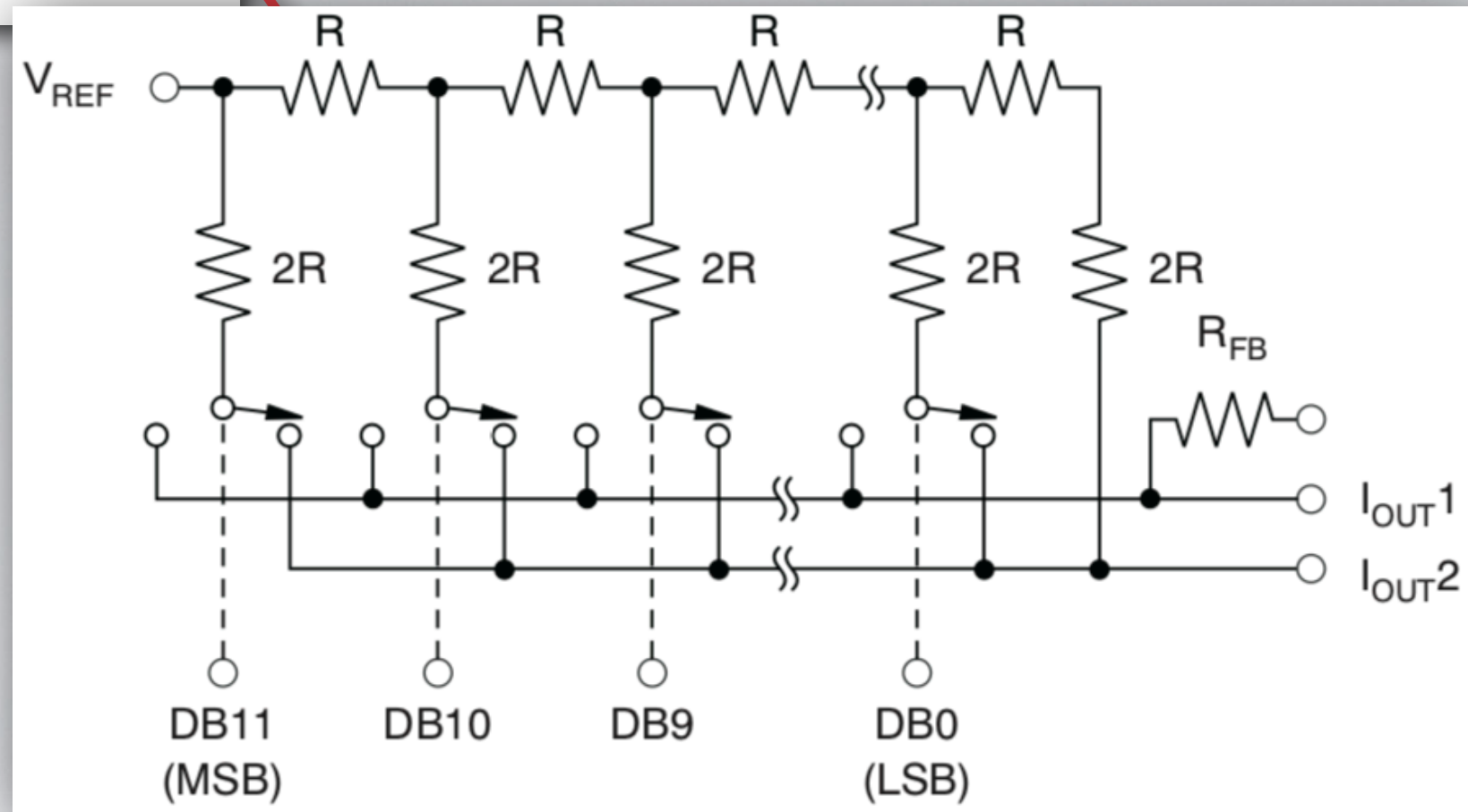


$$I_{out1} = \frac{V_{ref}}{R_{ges}} \cdot \frac{CODE}{2^{n_{Bits}}}$$

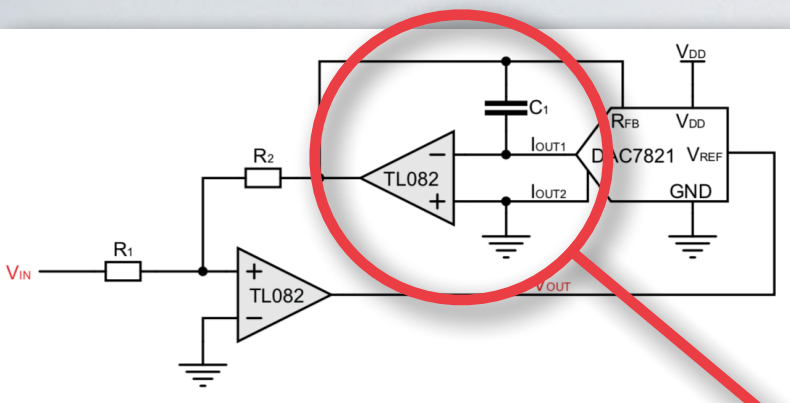DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER




Strom-Spannungswandler

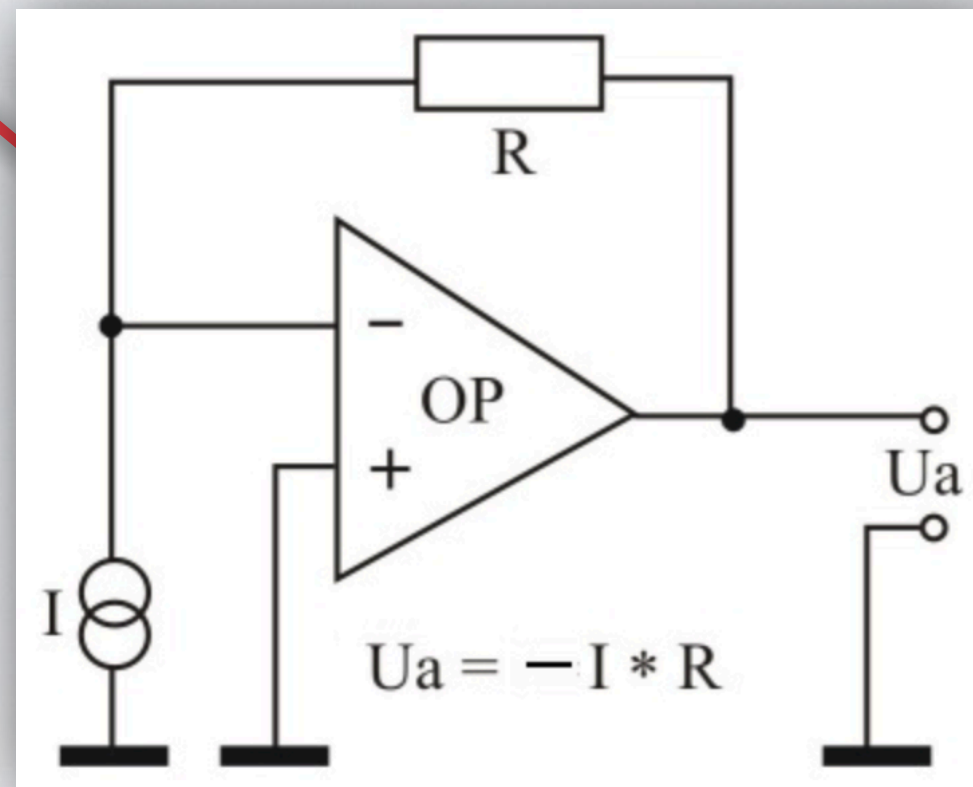


$$I_{out1} = \frac{V_{ref}}{R_{ges}} \cdot \frac{CODE}{2^{n_{Bits}}}$$

$$U_{out} = -\frac{V_{ref}}{R_{ges}} \cdot \frac{CODE}{2^{n_{Bits}}} \cdot R$$

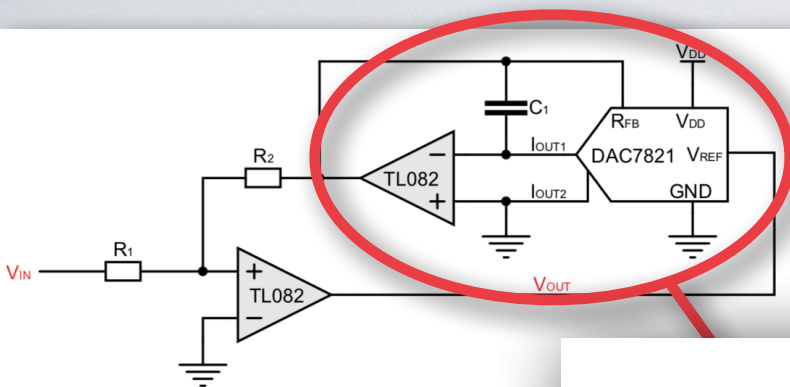DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER



Gaincontroller gesamt

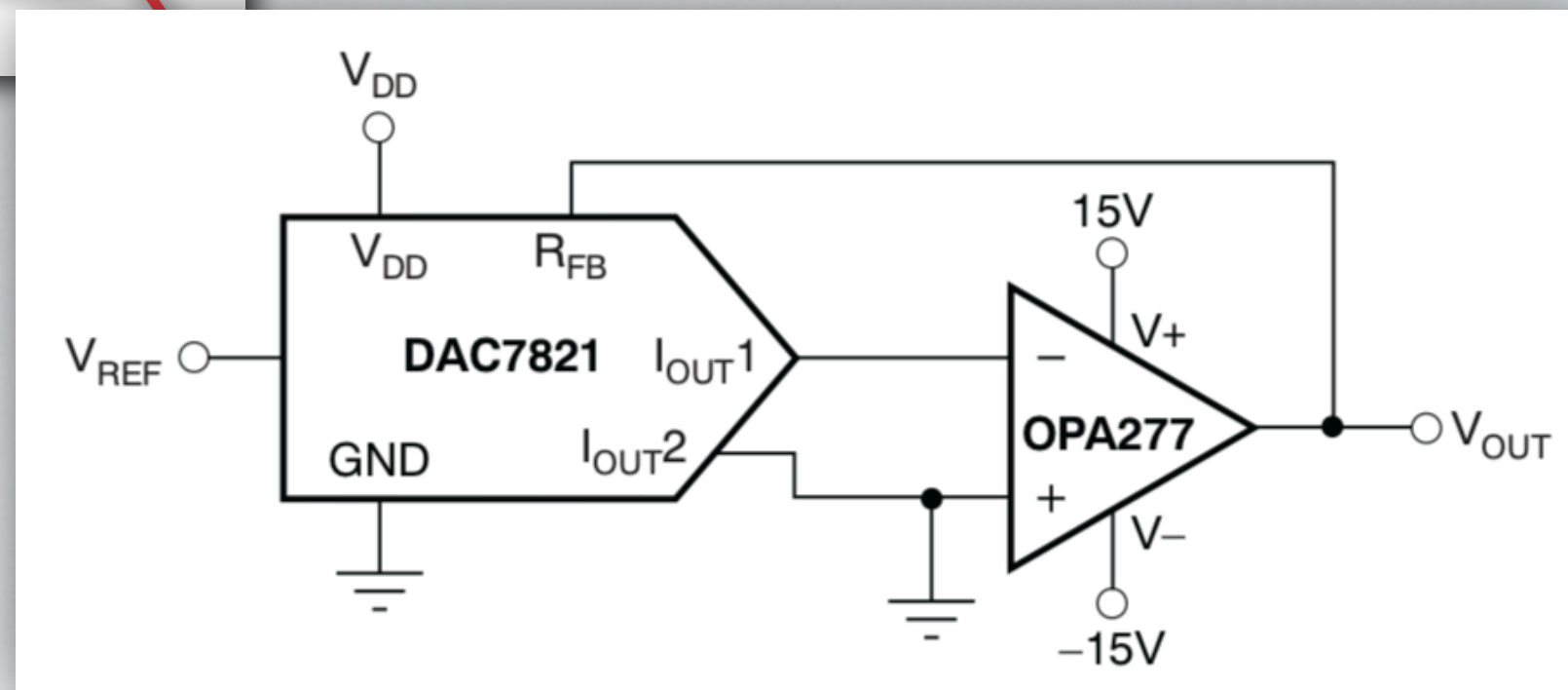


$$R_{ges} = R_{FB}$$



$$V_{out} = -V_{ref} \cdot \frac{CODE}{2^{n_{Bits}}}$$

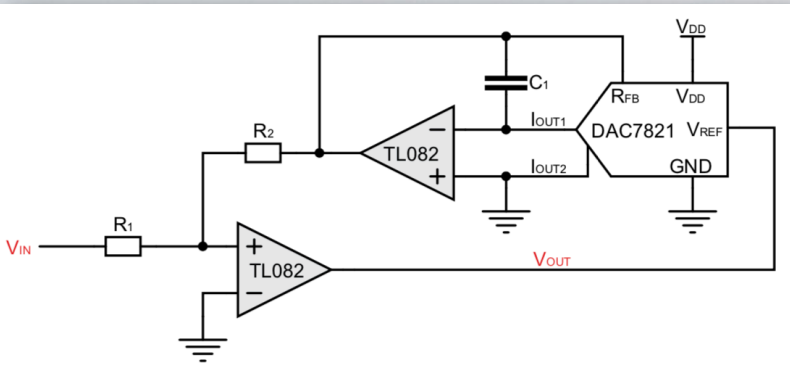DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER




Verstärker gesamt

$$\frac{V_{out}}{V_{in}} = \frac{R2}{R1}$$


$$\frac{V_{out} \cdot \frac{CODE}{2^n \text{ Bits}}}{V_{in}} = \frac{R2}{R1}$$
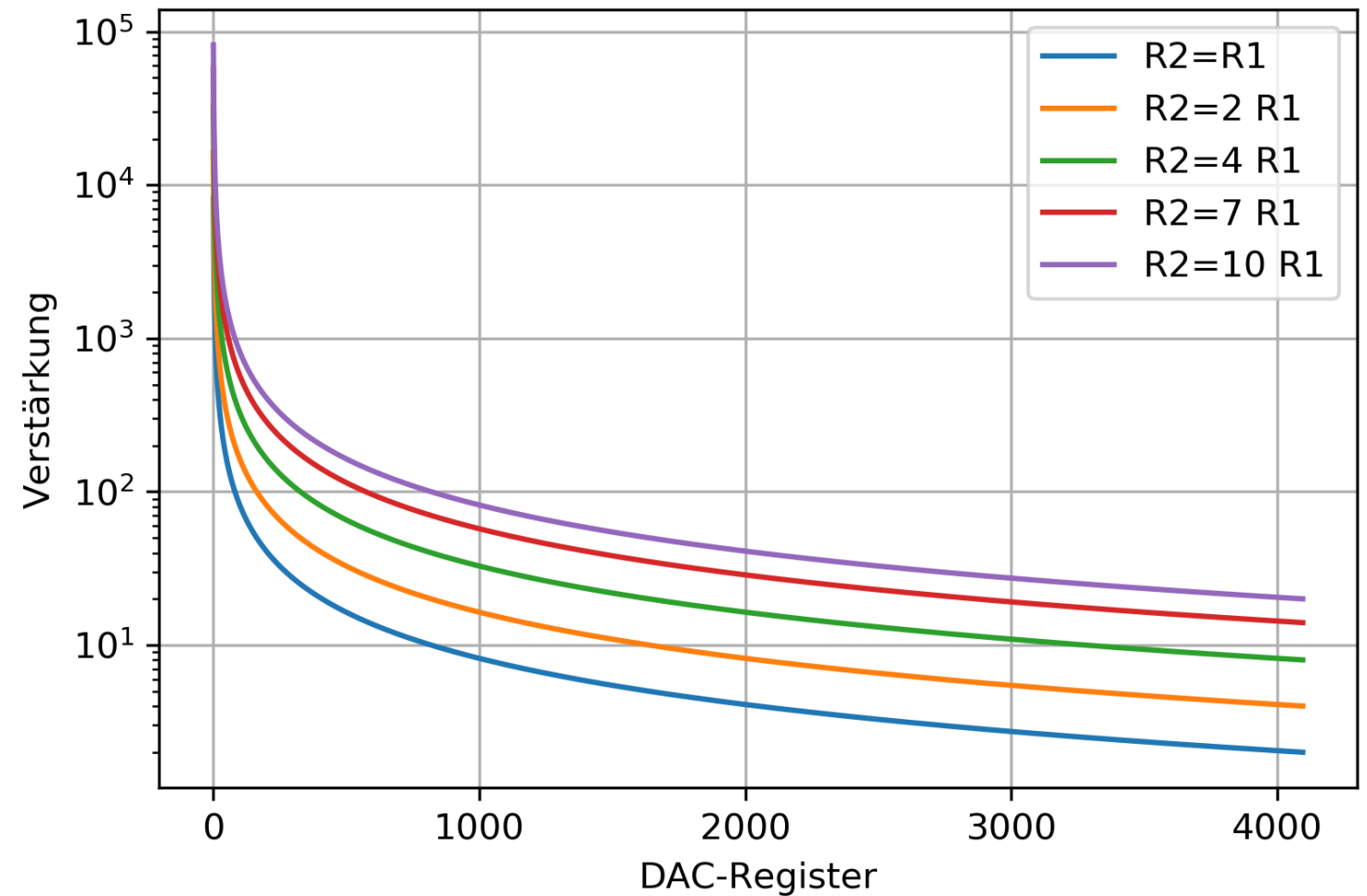
$$V_{out} = V_{in} \cdot \frac{R2}{R1} \cdot \frac{2^n \text{ Bits}}{CODE}$$




Verstärkungskennlinie Digitale Controller Main Stage Amplifier

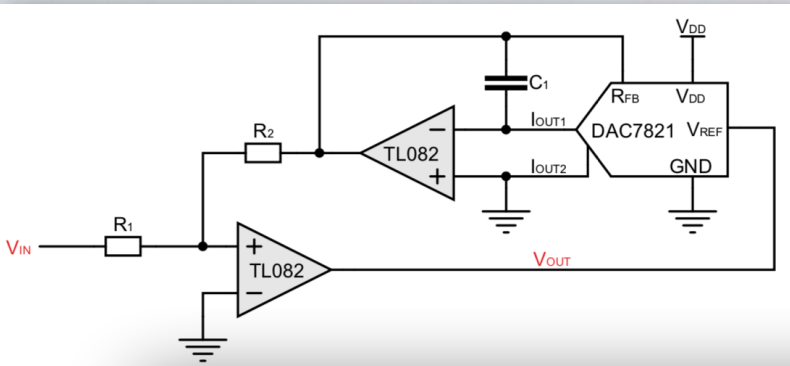
DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER



Simulation in LT Spice

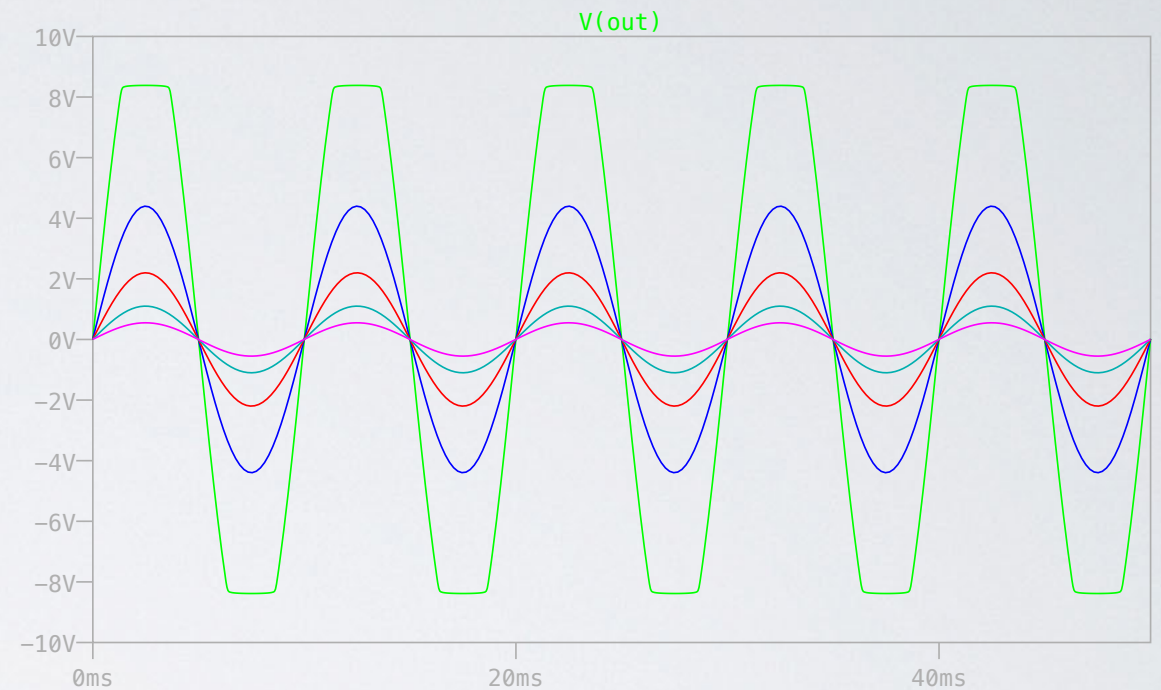


Zeitaufnahme Sinus bei 100Hz

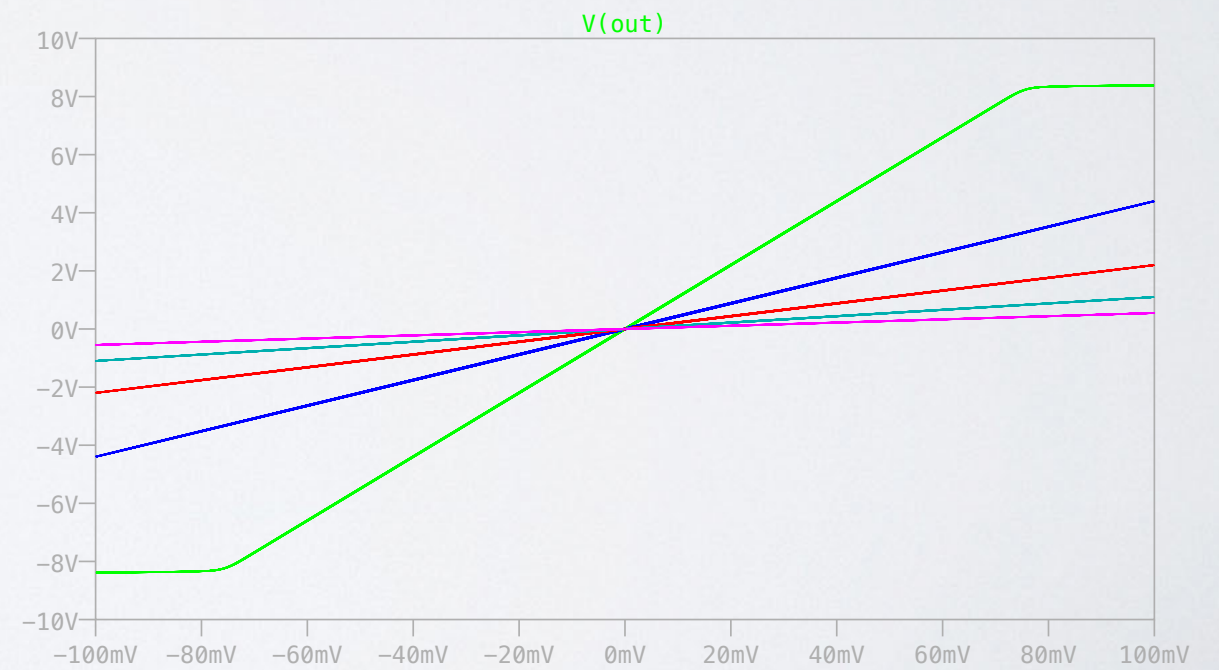

Verstärkungskennlinien Digitale Controller Main Stage Amplifier

DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER

Messung mit Experimentierboard

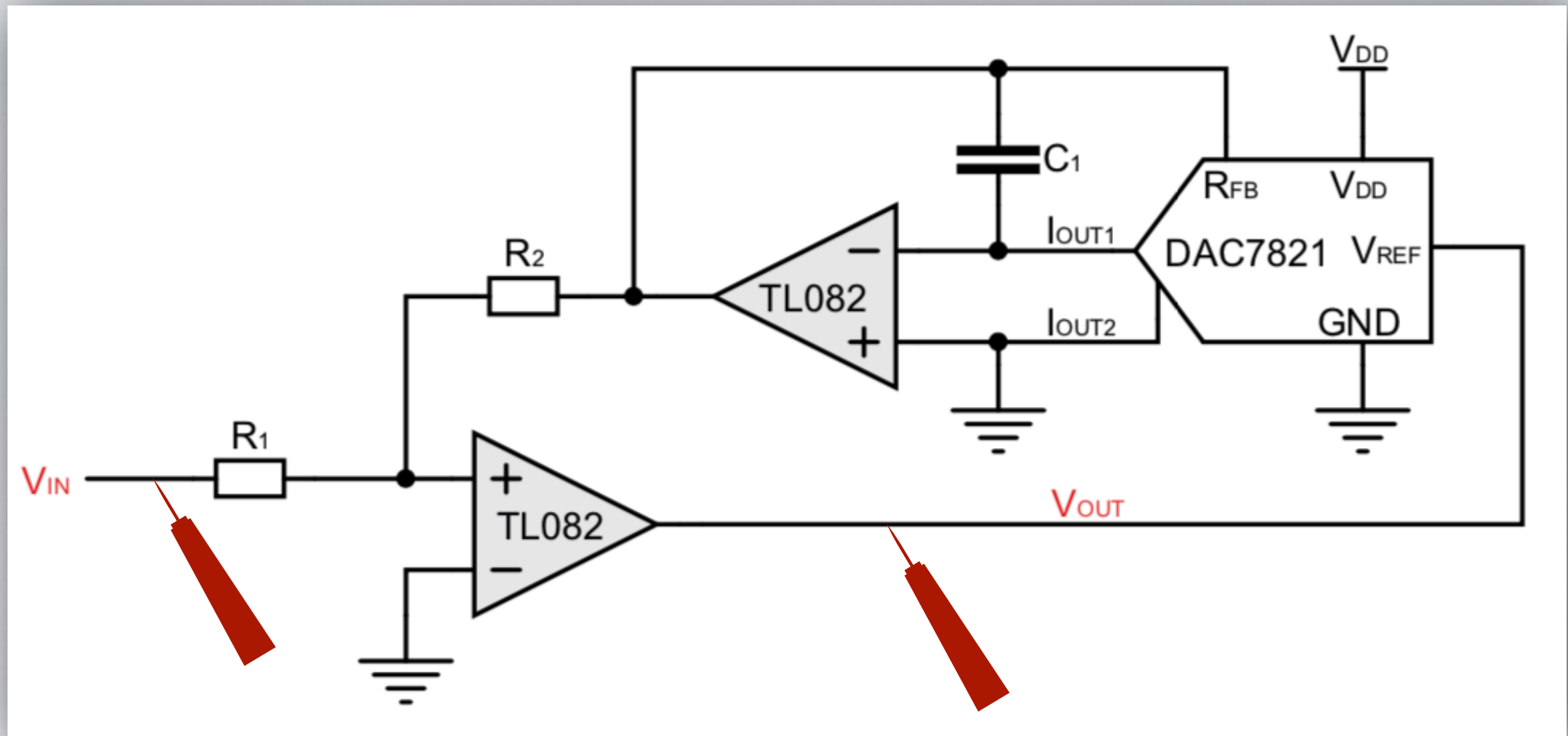


$$R_1 = 10k\Omega$$

$$R_2 = 22k\Omega$$


$$C_1 = 10nF$$

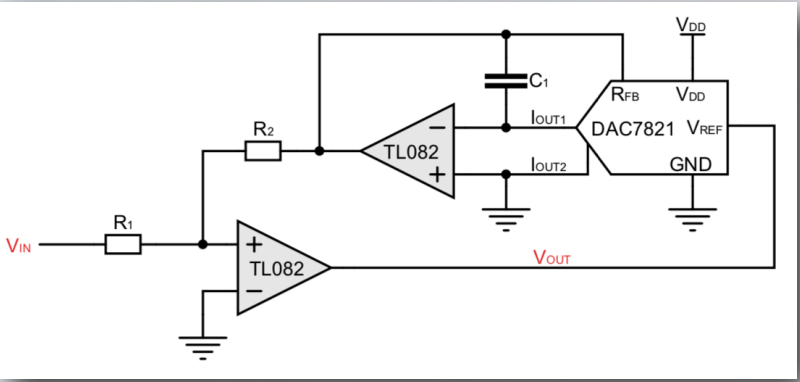DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER




$$\text{gain} = \frac{V_{out}}{V_{in}}$$

Messergebnis

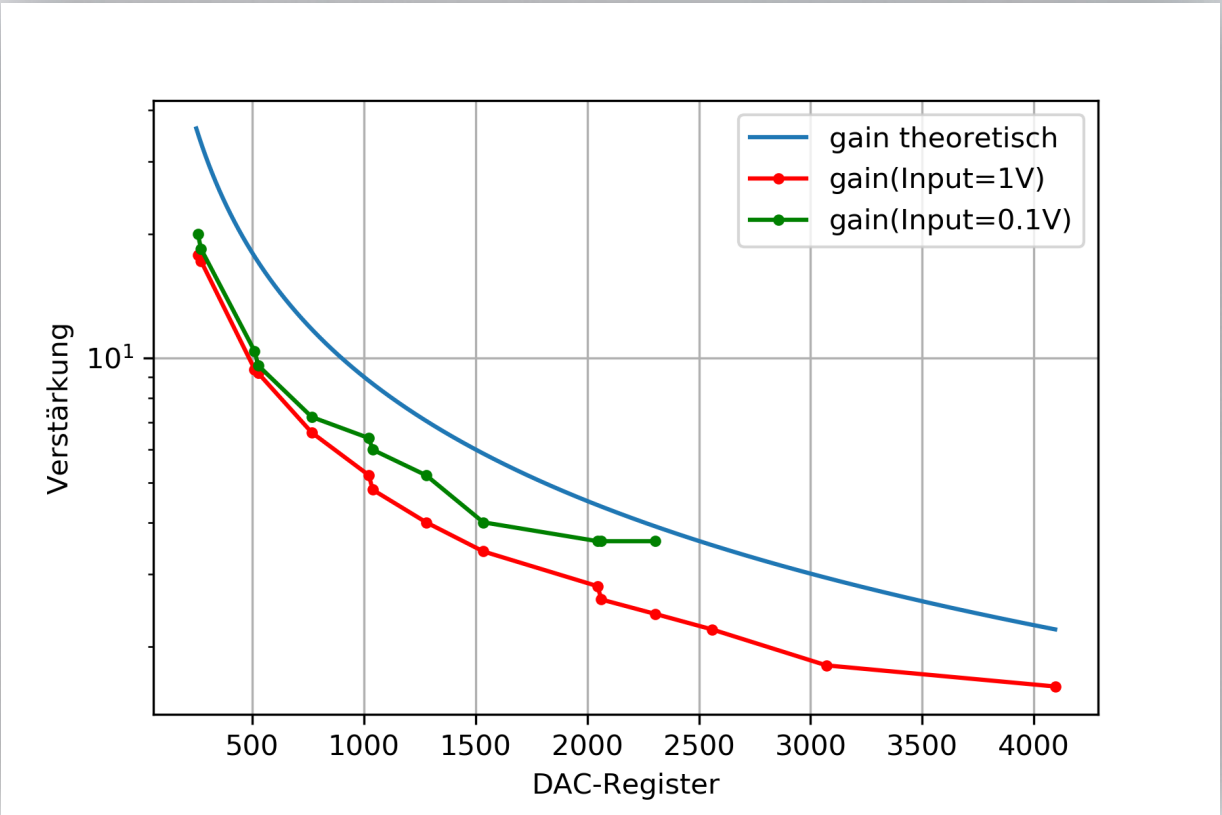


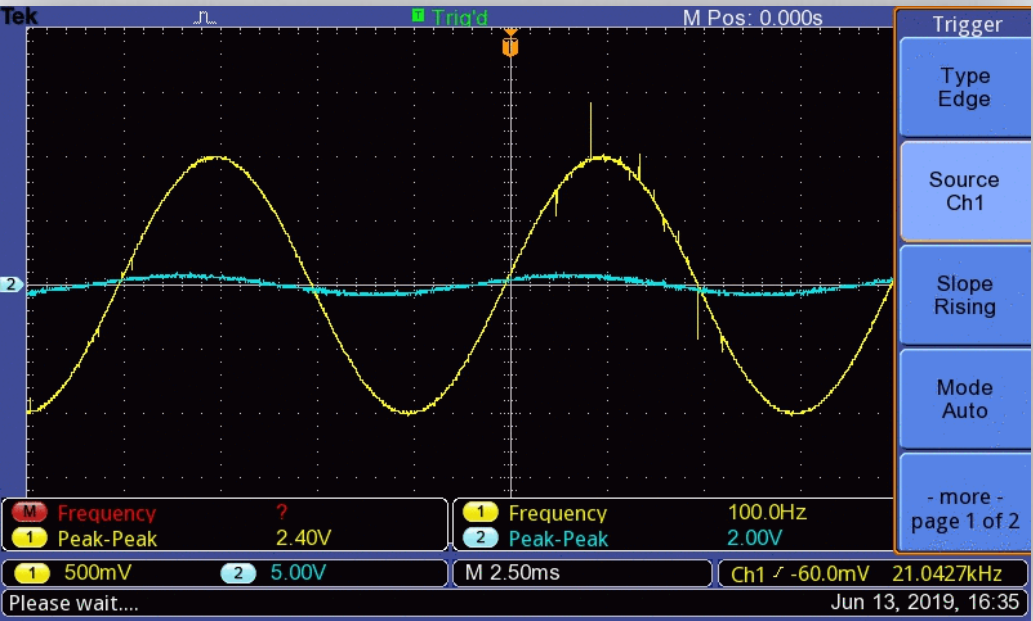Verstärkung Digitale Controller Main Stage Amplifier aus Messung



DIGITALLY CONTROLLED GAIN STAGE AMPLIFIER

Anmerkungen:

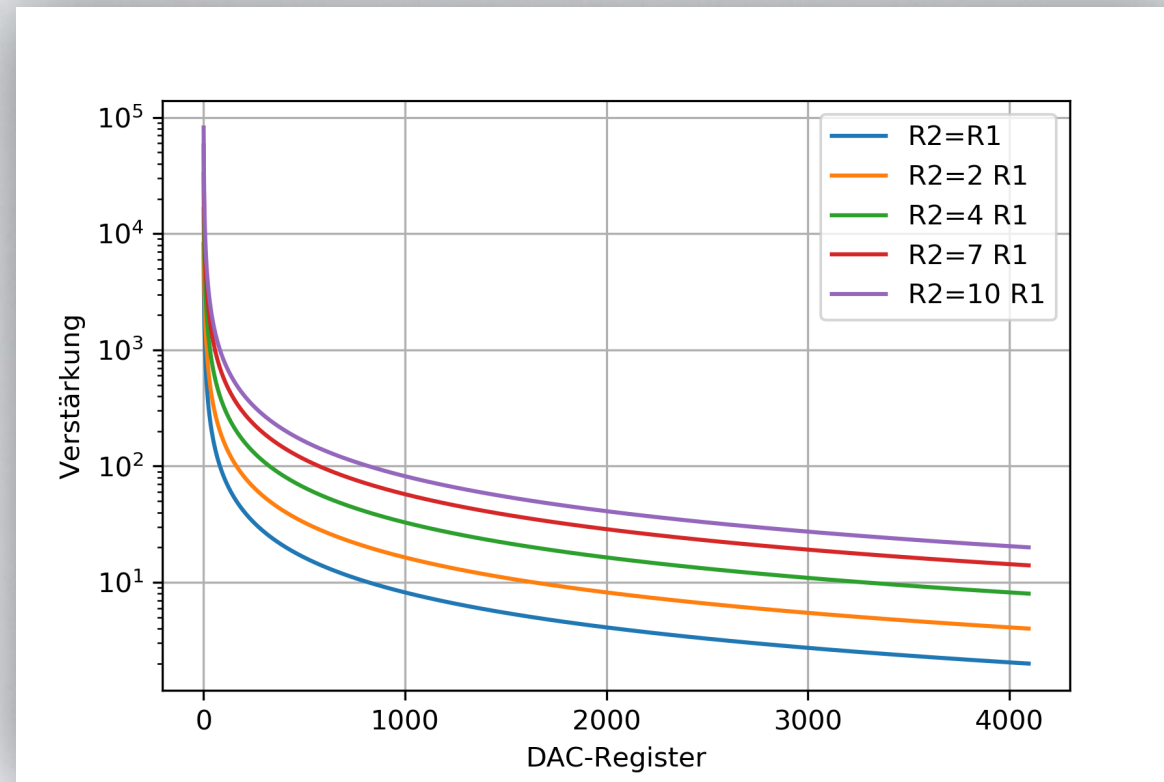

Sinnvoller Arbeitsbereich ~ 250 -4096